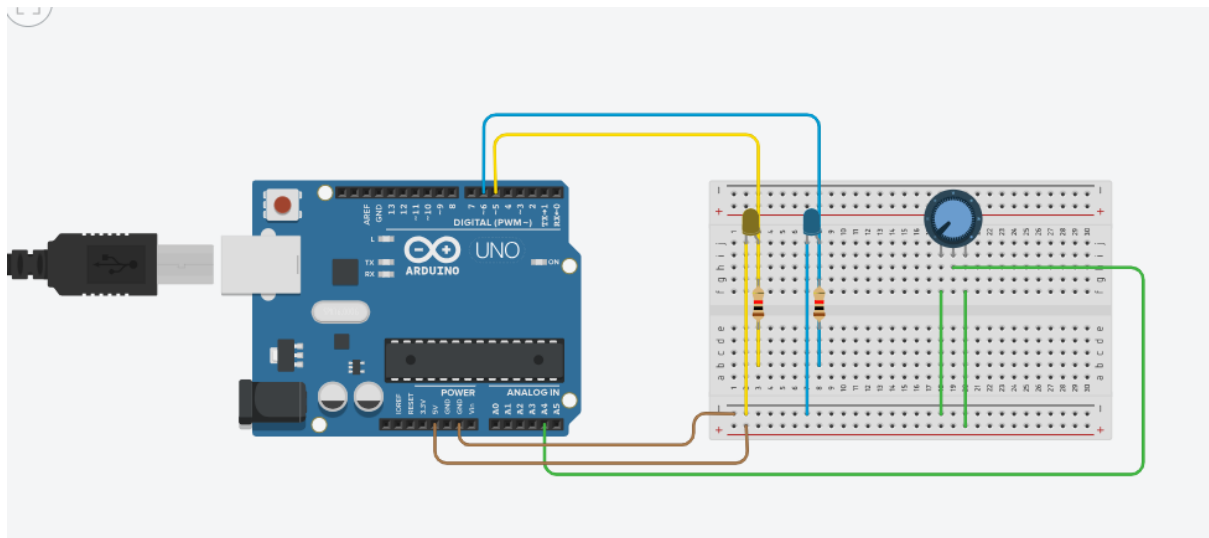


Robocon- Tinkercad Task-4.2

Circuit diagram and code explanation

Task-- TWO LEDs WITH POTENTIOMETER

Circuit:



Explanation:

Components used—Arduino UNO, breadboard, 2 LEDs, 2 Resistors, potentiometer, jumper wires

Code logic—

- We take input from potentiometer using `analogRead()` and store it in a variable(input)
- We use `map` function to convert the 10 bit input to 8 bit output
- As per the `map` value output of 1st LED is resulted and the remaining i.e $\text{max-maxvalue}(255\text{-value})$ is the output for LED2
- Print the values of potentiometer and LEDs output value using `Serial.print`