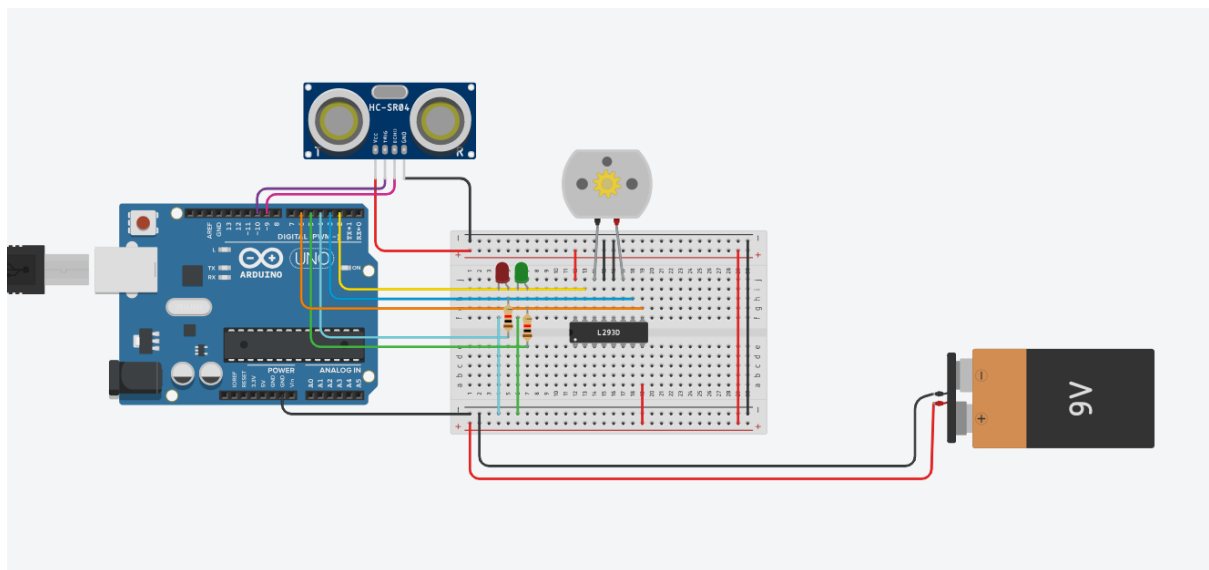


# Robocon- Tinkercad Major-Task

## Circuit diagram and code explanation

Task—To use different components in tinkercad to make sensible structure

Circuit:



Explanation:

Components used—Arduino UNO, DC motor, L293D, 2 LEDs, 2 resistors, USD, 9V battery, breadboard, jumper wires

Code logic—

- First USD will measure the distance of the object using trig and echo, and calculations
- Based on the distance if the distance is in between 20-60 then the red LED will glow and the motor will run at 50 bit
- If the distance is in between 60-200 then green LED will glow and motor will run at 100 bits

- If the distance is less than 20 and greater than 200 both LEDs turn off and motor is also off
- We print the distance and brightness of led for every loop