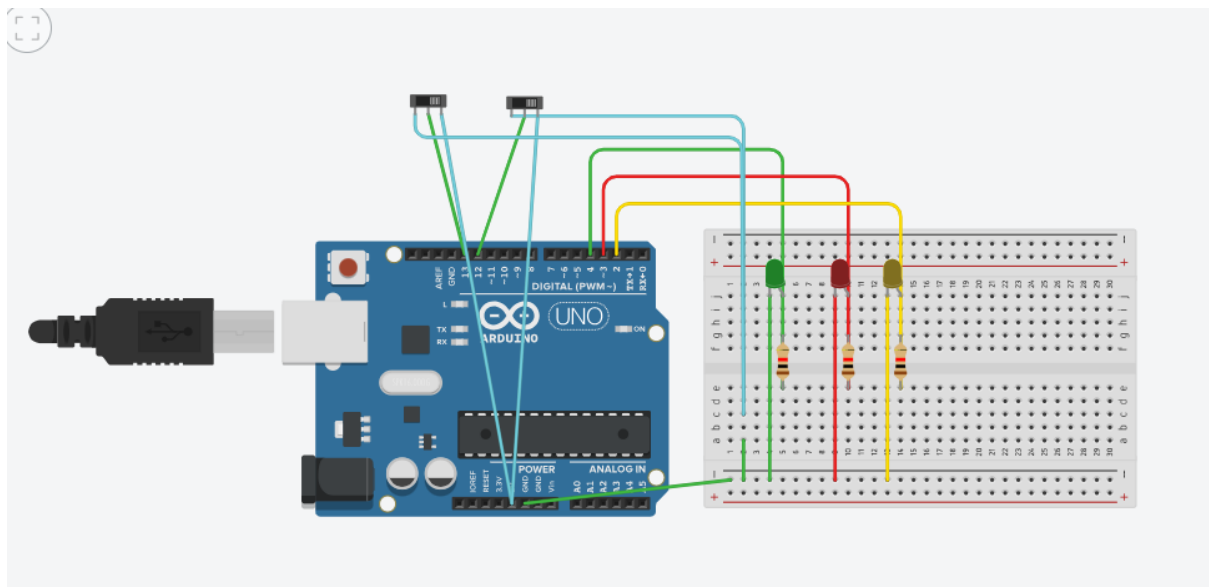


Robocon- Tinkercad Task 02

Circuit diagram and code explanation

Task- connect two switches and three LEDs to the Arduino and write a program that reads the state of both switches and controls the LEDs according to the given conditions

Circuit:



Explanation:

Components used—Arduino UNO, 3 LEDs, 3 resistors, 2 switches, jumper wires, breadboard

Code logic—

- We assign the pins to switches and LEDs and declare its pinmode
- To get the value (0/1) correspondingly turning the switch off/on we use `digitalRead()` in whose argument we mention the switch and store the value in a variable

- Use if else condition to change LED status depending on the input from switches
 - Both switches on/1 green LED glows rest two are off
 - 1st switch is off and 2nd switch is on then red LED glows and the other two are off
 - If 2nd switch is off irrespective of the first switch's status yellow LED glows and the rest two are at rest/off