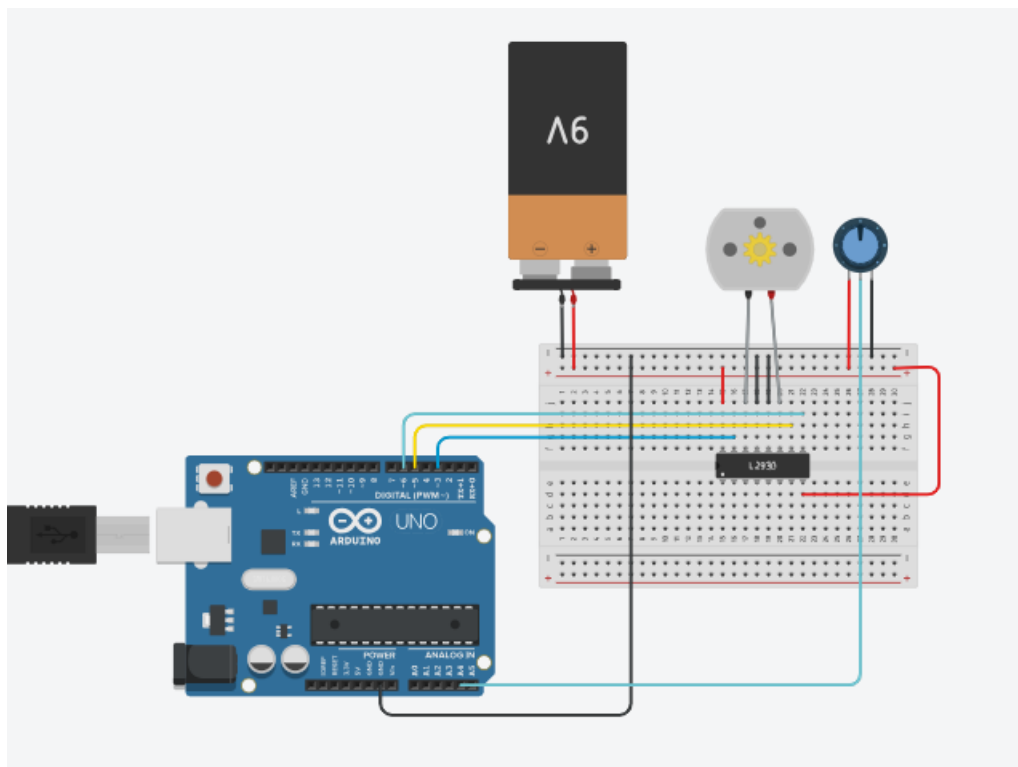


Robocon- Tinkercad Task-5

Circuit diagram and code explanation

Task— Control the speed of a DC motor using a potentiometer and L293D motor driver

Circuit:



Explanation:

Components used—Arduino UNO, DC motor, potentiometer, 9V battery, L293D motor driver, breadboard, jumper wires

Code logic—

- We take the analog input of potentiometer
- Use map function to convert the potentiometer value into 8-bit output

- For one direction we keep one path high and other low and give the enable the converted output value of potentiometer
- For other direction we just switch the high and low pins